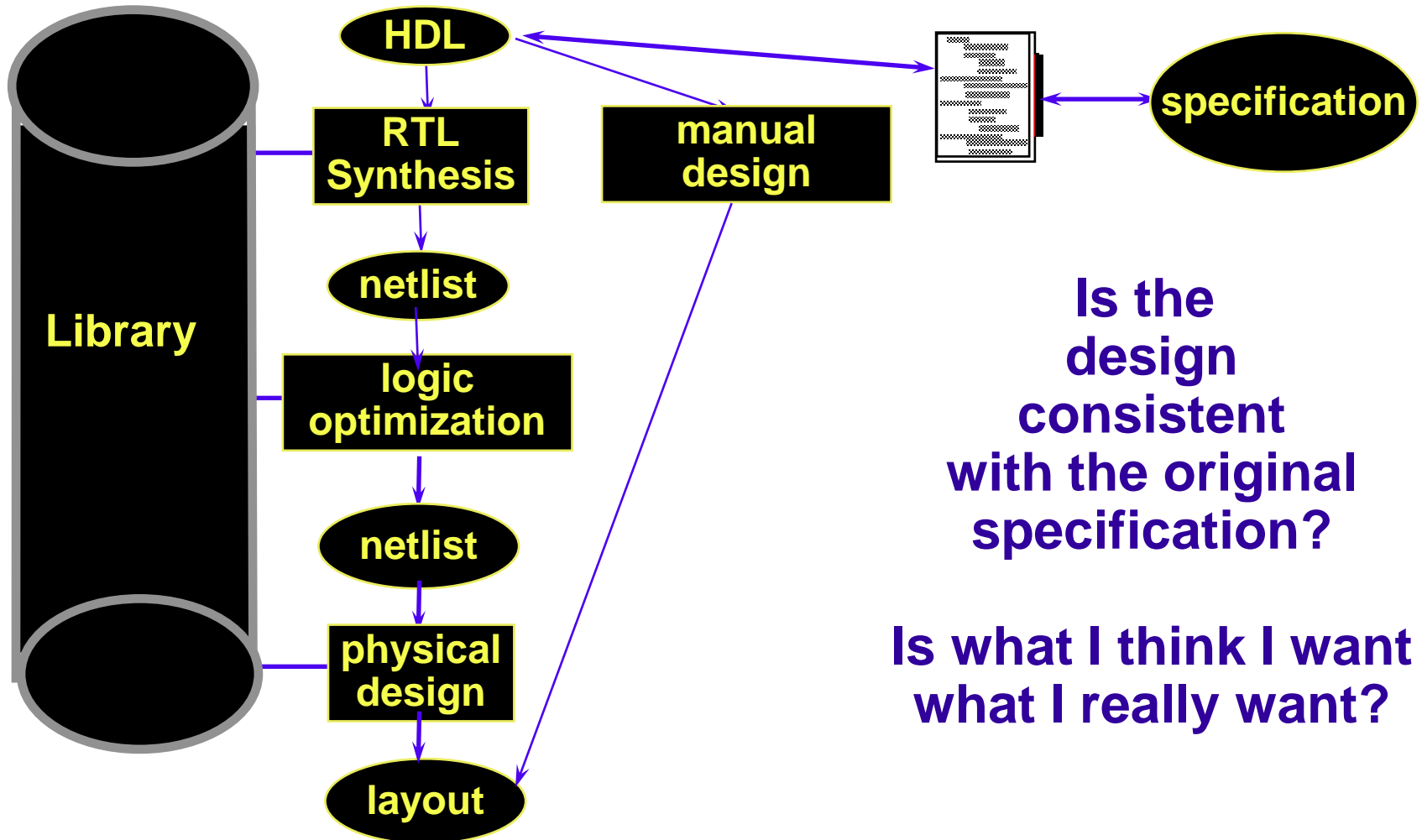



# **Manufacture Testing of Digital Circuits**

**Alexander Gnusin**


# Design Verification



# Implementation Verification

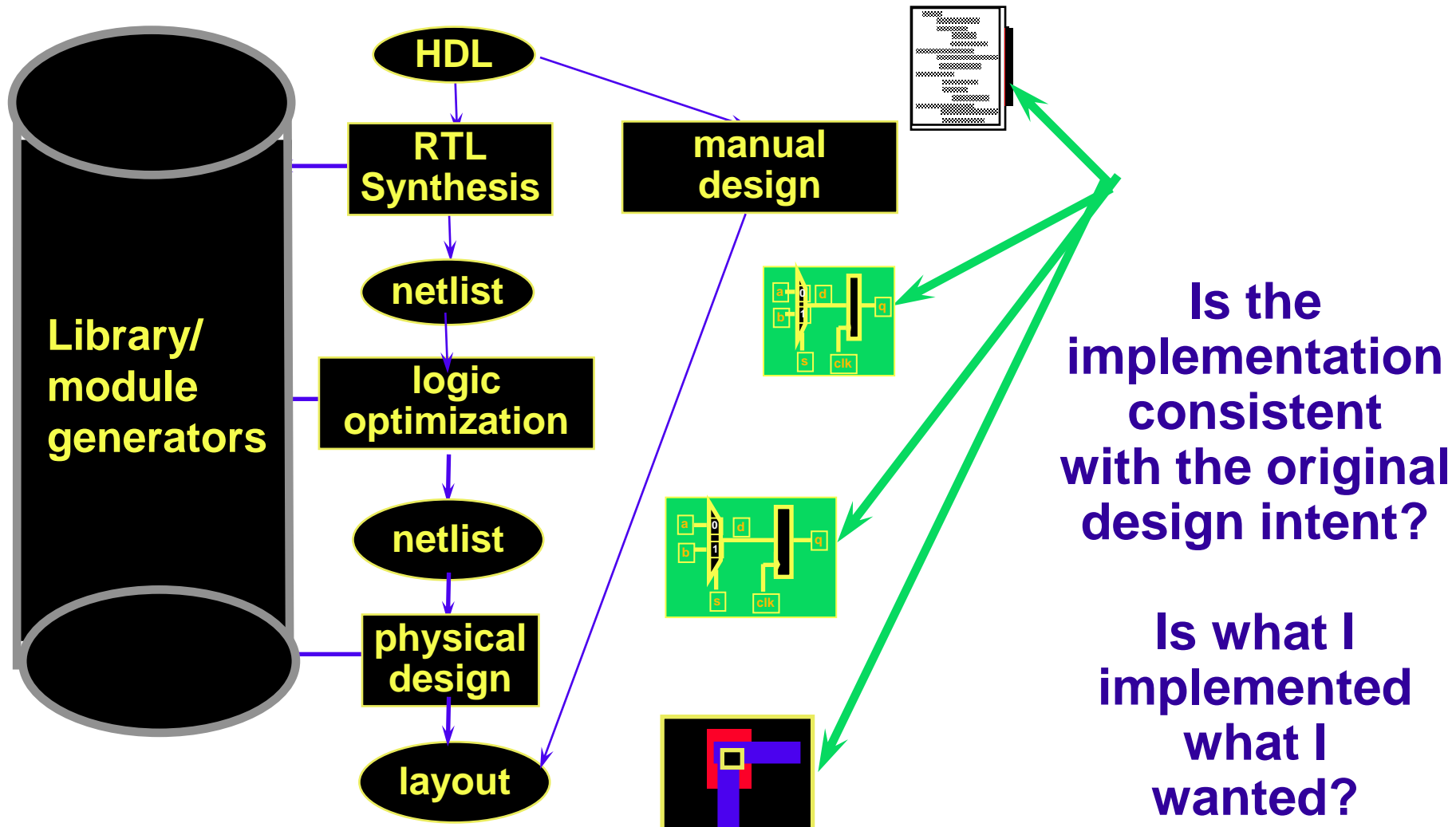


# Manufacture Verification (Test)

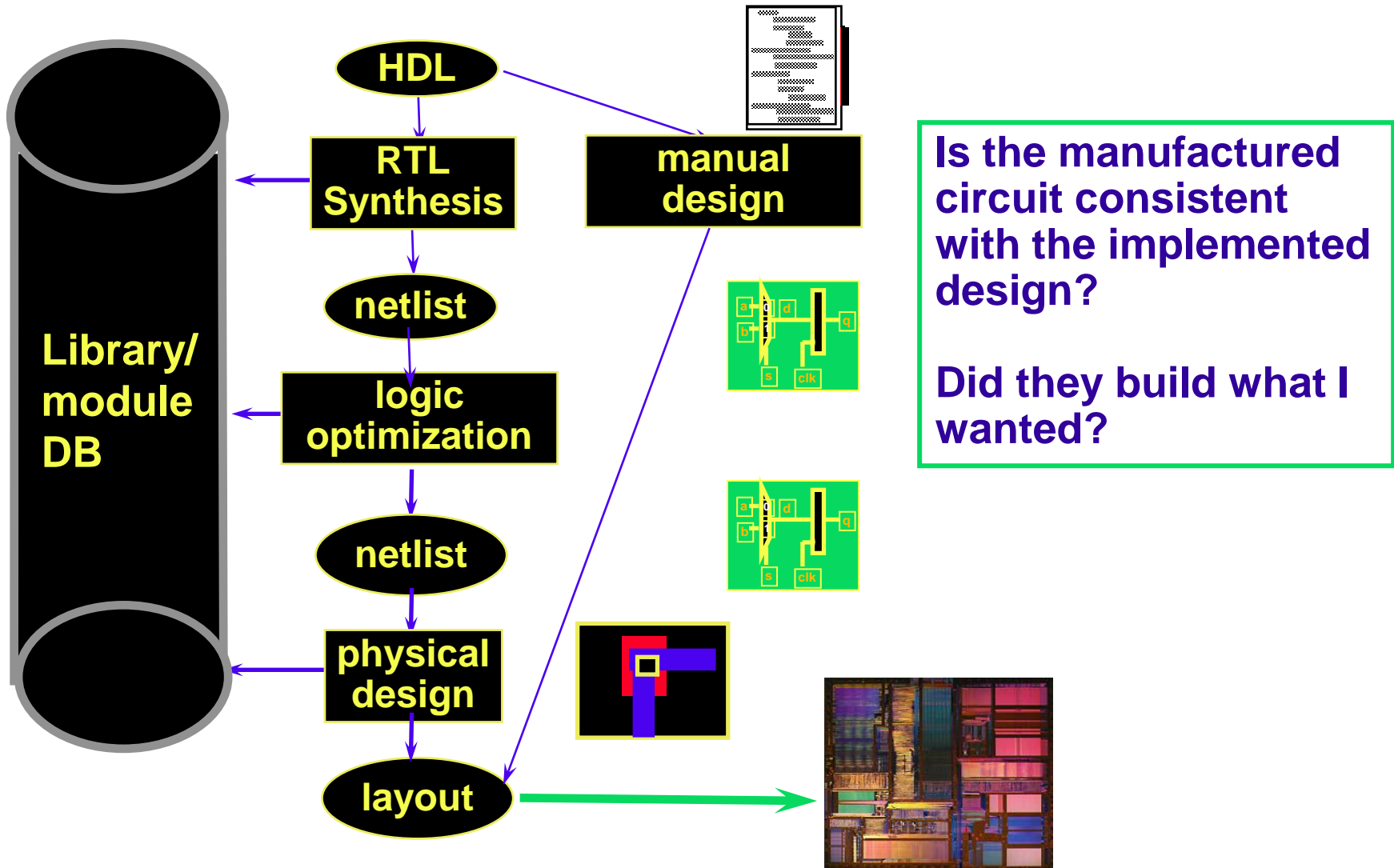

# Defects and Fault models

 
## Types of Manufacturing defects:

- Bridging (1)
- Shorts (2)
- Opens (3)
- Transistors stuck-open (4)



 
## These need to be reduced to models:


- Single stuck-at-1, stuck-at-0
- Multiple stuck-at-1, stuck-at-0
- Delay fault models:
  - Gate
  - Path



# Fault Models

 


 **Single stuck-at fault:**  
 In the faulty circuit, a single line/wire is S-a-0 or S-a-1




**Multiple stuck-at faults:**  
 In the faulty circuit any subset of wires are S-a-0 or S-a-1 (in any combination)

# Fault Models - 2

 

Gate delay fault

 

Path delay fault


# Sequential to Combinational Logic reduction

Internal scan chains: add additional state to flip-flops  
(15 - 20% area overhead)

TE = 0 : Functional mode, no influence

TE = 1 : Scan mode, any data can be loaded/extracted

 Data Input of FF acts as additional Primary Output  
The Output of FF acts as additional Primary Input





# Test Generation

Choose a fault model, e.g., single stuck-at fault model

Given a combinational circuit which realizes the function  $f(x_1, x_2, \dots, x_n)$ , a logical fault changes it to  $f_{\infty}(x_1, x_2, \dots, x_n)$



Inputs detecting  $\infty$  are  $f \oplus f_{\infty} (= 1)$

Interested in one vector

$$A = (a_1, a_2, \dots, a_n) \in f \oplus f_{\infty}$$
  
# Single Stuck-At Faults

A fault is assumed to occur only on a single line.



# Definitions

Controlability of internal point  $x$ : exist input vectors  $V0\{x\}$  and  $V1\{x\}$  that set  $x$  to 0 and 1


Observability of internal point  $x$ : exist input vector  $V_{obs}\{x\}$  that drives the value of  $x$  to primary output

Cofactors of function  $F(x,y,z)$  w.r.t. variable  $x$ :

$$F_x = F(1,y,z), F_{\bar{x}} = F(0,y,z)$$

Shannon Expansion of function  $F(x,y,z)$ :
 
$$F(x,y,z) = x * F_x + \bar{x} * F_{\bar{x}}$$



# Boolean Difference

Circuit C has function  $f(x_1, x_2, \dots, x_n)$

Input  $x_i$  s-a-0 (fault  $\infty$ )


$$f_{\infty} = f_{\bar{x}_i} \text{ (cofactor of } f \text{ w.r.t. } \bar{x}_i)$$

Set of tests detecting  $\infty$

$$\begin{aligned} T &= f \oplus f_{\infty} \\ &= (x_i f_{x_i} + \bar{x}_i f_{\bar{x}_i}) \oplus f_{\bar{x}_i} \\ &= x_i (f_{x_i} \oplus f_{\bar{x}_i}) \end{aligned}$$

$$\frac{df}{d\bar{x}_i} = f_{x_i} \oplus f_{\bar{x}_i} \text{ - Boolean difference of } f \text{ w.r.t. } x_i$$

# Boolean Difference Example

 

$$\text{Function: } f = (x_2 + x_3)x_1 + x_1 x_4$$

**$x_1$  s-a-0** - compute  $x_1 \frac{df}{dx_1}$

$$\frac{df}{dx_1} = f(0, x_2, x_3, x_4) \oplus f(1, x_2, x_3, x_4)$$

$$= x_4 \oplus (x_2 + x_3)$$

$$T = x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 + x_1 x_2 \bar{x}_4 + x_1 x_3 \bar{x}_4$$

# Internal Faults

Let  $C$  be a circuit for  $f(X)$  and  $h$  be an internal signal in  $C$ .

Represent  $h$  as a Boolean function  $h(X)$


Express  $f$  as a function of inputs  $X$  and  $h$

$$f^*(X, h) \equiv f(X)$$

Set of all tests for  $h$  s-a-0

$$h(X)^* \frac{df^*(X, h)}{dh}$$

# Internal Faults Example

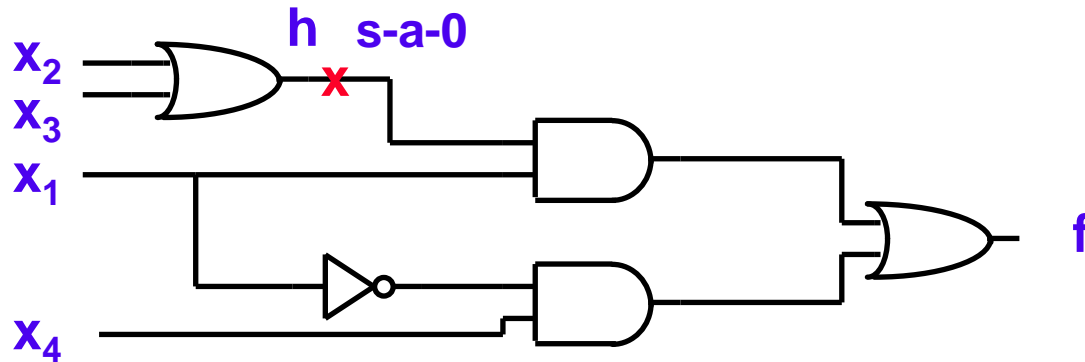

$$f = (x_2 + x_3)x_1 + \bar{x}_1 x_4$$


$$f^* = h x_1 + \bar{x}_1 x_4 \quad h = x_2 + x_3$$

$$\begin{aligned} \frac{df^*}{dh} &= f^*(x_1, x_4, 0) \oplus f^*(x_1, x_4, 1) \\ &= \bar{x}_1 x_4 \oplus (x_1 + \bar{x}_1 x_4) = x_1 \end{aligned}$$

Result :  $T = x_1 x_2 + x_1 x_3$
 
# Path Sensitization

In order for an input vector  $X$  to detect a fault  $a$  s-a-j,  $j = 0,1$  the input  $X$  must cause the signal  $a$  in the normal (fault-free) circuit to take the value  $j$ .




The condition is necessary but not sufficient.  
Error signal must be propagated to output.


 
# Error Propagation

The error signal must be propagated along some path from its origin to an output



$h$  s-a-1, for  $h$  to be  $0$ , need  $x_2 = x_3 = 0$  ( $\overline{x_2} \overline{x_3}$ )


Only one path  $G_3, G_5$

In order to propagate an error through AND gate  $G_3$ , other input  $x_1 = 1$ . To propagate through  $G_5$ , need  $G_4 = 0, x_1 + \overline{x_4}$

# Single Path Sensitization (SPS)

1. Specify inputs so as to generate the appropriate value (0 for s-a-1, 1 for s-a-0) at the site of the fault.
2. Select a path from the site of the fault to an output and specify additional signal values to propagate the fault signal along this path to the output (**Error propagation**).
3. Specify input values so as to produce the signal values specified in (2) (**Line justification**).

# Sensitization Example

 

h s-a-1

To generate  $h = 0$ , we need  $A = B = C = 1$

Have a choice of propagating through  $G_5$  or via  $G_6$ .

Propagating through  $G_5$  requires  $G_2 = 1$


$\Rightarrow A = D = 0$ , **Contradiction**

Propagating through  $G_6$  requires  $G_4 = 1 \Rightarrow C = 1, E = 0$ .

A valid test vector is **ABC $\bar{E}$**
 
# Redundancy

Existence of a fault does not change the functionality of a circuit  $\Rightarrow$  redundant fault




A test generation algorithm is assumed complete if it either finds a test for any fault or proves its redundancy, upon terminating.
 
# Implementation Verification and Testing

Given two single-output circuits A and B

Are A and B equivalent can be posed as: Is there a test for F s-a-0?




If F s-a-0 is redundant,  $A \equiv B$  else test vector produces different outputs for A and B.

# Implementation Verification (cont)


## 2 Stages of functional verification:

- Match Primary Input, Primary Output and Register names between two designs
- Check Functional Equivalence of each one of matching logic cones

**Design A**

 


**Design B**

 
 
## Usage of Shannon expansion for Timing Optimization

$$F(x,y,z) = x * F_x + \bar{x} * F_{\bar{x}}$$



**Problem: Long Timing Path from input A to output Y**  
**Solution: Use Shannon expansion of Y by A:**

